





Government of Karnataka
Karnataka School Examination and Assessment Board
II Year PUC Examination March – 2023
SCHEME OF VALUATION

Subject Code: **40(NS)**

Subject: **ELECTRONICS**

I	PART - A	MARKS
MCQ		15x1 =15
1. c)	Gate	1
2. b)	Voltage Divider biasing	1
3. a)	180 ⁰	1
4. b)	Amplifier	1
5. b)	Infinity	1
6. c)	Cosine Wave	1
7. d)	AB = 1	1
8. b)	Transmitter	1
9. d)	Infinity	1
10. d)	LED	1
11. a)	Pair	1
12. a)	Half Adder	1
13. a)	8 bit	1
14. c)	Logical AND	1
15. d)	4 GHz	1
II	FILL THE BLANKS	5x1 = 5
16. d)	Input impedance	1
17. e)	Heat sink	1
18. c)	RC coupled	1
19. b)	Modulation index	1
20. a)	Data	1

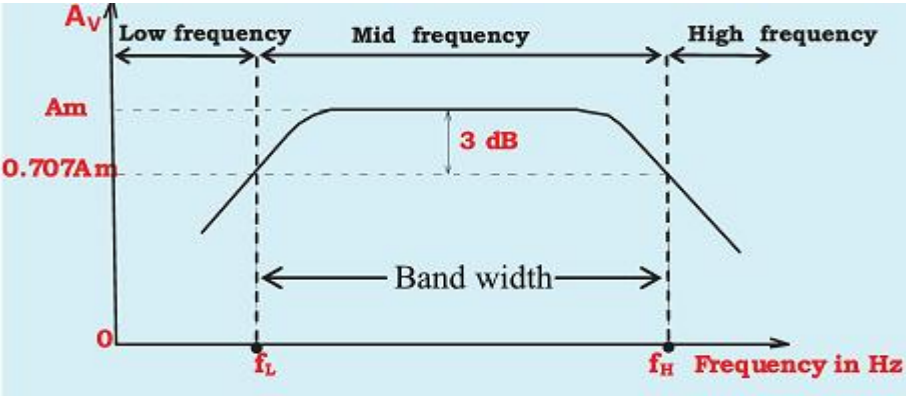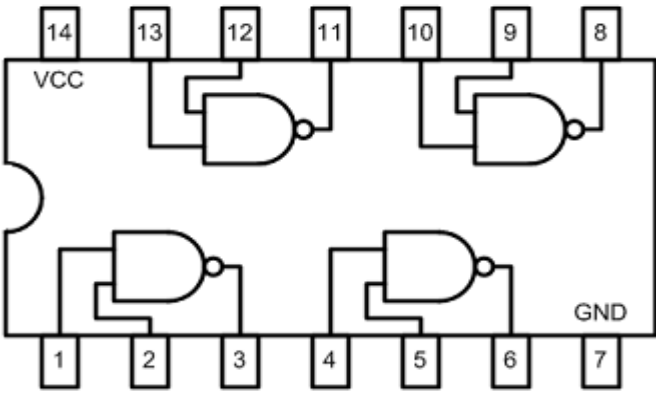III.	PART B	5x2 = 10
21.	<p>Any five of the following</p> <p>Collector Base leakage current when Emitter is kept open (or) I_{CBO}</p> <p>Collector Emitter leakage current when Base is kept open (or) I_{CEO}</p>	<p>1</p> <p>1</p>
22.	 <p>Nature of Curve</p> <p>Marking regions</p>	<p>1</p> <p>1</p>
23.	$A_{vf} = \frac{A_v}{1+A_v\beta} \quad A_v = 500, A_{vf} = 100$ $\beta = \frac{1}{A_f} - \frac{1}{A}$ $= \frac{1}{100} - \frac{1}{500}$ $\beta = 0.008 \quad (\text{or}) \quad 0.8\%$	<p>1</p> <p>1</p>
24.	$f = 78\text{Hz}, C = 220\text{nF}, R = ?$ $f = \frac{1}{2\pi RC\sqrt{6}} \text{ or } \frac{0.065}{RC}$ $R = \frac{1}{2 \times 31.42 \times \sqrt{6} \times 78 \times 220 \times 10^{-9}} = 3.785\text{k}\Omega$	<p>1</p> <p>1</p>
25.	<p>i). Rectifier</p> <p>ii). AC Voltage controller</p> <p>iii). DC Chopper</p> <p>iv). Inverter</p> <p style="text-align: right;">(Any two each 1M)</p>	<p>1</p> <p>1</p>
26.	 <p style="text-align: right;">(Pin Numbers)</p>	<p>1</p> <p>1</p>
27.	<p>ALU : This unit does the arithmetic operations and also does the logical decisions</p> <p>Accumulator: it is a device which stores a number and which on receipt of another number, adds the two stored sum. (or) it is an intermediate storage of arithmetic and logical data in CPU (or) 8 bit dedicated default storage register which is a part of ALU.</p>	<p>1</p> <p>1</p>

28.	Syntax error Logical error Runtime error <p style="text-align: right;">(Any two)</p>	1 1								
29.	Any two advantages of digital cell phone system. (each 1M)	2								
IV 30.	PART C Any five of the following Working of n-channel JFET Diagram Case 1($V_{GS} = 0$)- (effect) Case 2(V_{GS}) is increased	5x2 = 10 1 1 1								
31.	Any three difference between positive and negative feedback (each 1 M) <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%; text-align: center;">Positive feedback</th> <th style="width: 50%; text-align: center;">Negative feedback</th> </tr> </thead> <tbody> <tr> <td>It is Regenerative feedback, gain increases</td> <td>It is Degenerative feedback, gain decreases</td> </tr> <tr> <td>Feedback signal is INPHASE with source signal $V_i = V_s + V_f$</td> <td>Feedback signal is OUT OF PHASE with source signal $V_i = V_s - V_f$</td> </tr> <tr> <td>Suitable for oscillator</td> <td>Suitable for Amplifier</td> </tr> </tbody> </table>	Positive feedback	Negative feedback	It is Regenerative feedback, gain increases	It is Degenerative feedback, gain decreases	Feedback signal is INPHASE with source signal $V_i = V_s + V_f$	Feedback signal is OUT OF PHASE with source signal $V_i = V_s - V_f$	Suitable for oscillator	Suitable for Amplifier	3
Positive feedback	Negative feedback									
It is Regenerative feedback, gain increases	It is Degenerative feedback, gain decreases									
Feedback signal is INPHASE with source signal $V_i = V_s + V_f$	Feedback signal is OUT OF PHASE with source signal $V_i = V_s - V_f$									
Suitable for oscillator	Suitable for Amplifier									
32.	Any three comparison between RC and LC oscillators (each 1 M) <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%; text-align: center;">RC Oscillators</th> <th style="width: 50%; text-align: center;">LC oscillators</th> </tr> </thead> <tbody> <tr> <td>Resistors and capacitors are used in feed back circuit</td> <td>Inductors and capacitors are used in feedback circuit</td> </tr> <tr> <td>Generates low frequency signal</td> <td>Generates high frequency signals</td> </tr> <tr> <td>Examples are phase shift oscillators and wein bridge oscillators</td> <td>Examples are Hartley and colpitt's oscillators</td> </tr> </tbody> </table>	RC Oscillators	LC oscillators	Resistors and capacitors are used in feed back circuit	Inductors and capacitors are used in feedback circuit	Generates low frequency signal	Generates high frequency signals	Examples are phase shift oscillators and wein bridge oscillators	Examples are Hartley and colpitt's oscillators	3
RC Oscillators	LC oscillators									
Resistors and capacitors are used in feed back circuit	Inductors and capacitors are used in feedback circuit									
Generates low frequency signal	Generates high frequency signals									
Examples are phase shift oscillators and wein bridge oscillators	Examples are Hartley and colpitt's oscillators									
33.	$L_1 = 4\text{mH}$, $L_2 = 2\text{mH}$ and $C = 10\text{nC}$, $f = ?$ $f = \frac{1}{2\pi\sqrt{L_T C}}$ where $L_T = L_1 + L_2$ $= \frac{1}{2 \times 3.142 \times \sqrt{(2 \times 10^{-3} + 4 \times 10^{-3}) \times 10 \times 10^{-9}}}$ $= 20.544$	2 1								
34.	Any three waves with meaning (or brief explanation on each wave) (each 1 M) Ground wave Sky wave Space wave etc	1 1 1								
35.	Need for modulation (any three points with brief explanation) (each 1 M)	3								

36. $\alpha = 60^\circ, V_{\text{rms}} = 230\text{V}, R = 25\Omega$


$V_{\text{rms}} = \sqrt{2}V_{\text{rms}} = 385.5$

$V_{\text{dc}} = \frac{V_m}{\pi} [1 + \cos \alpha] = \frac{325.2}{3.142} [1 + \cos(60)]$
 $= 155.25\text{V}$

$I_{\text{dc}} = \frac{V_{\text{dc}}}{R} = \frac{155.25}{25} = 6.21\text{A}$

1
1
1

37. Logic circuit diagram

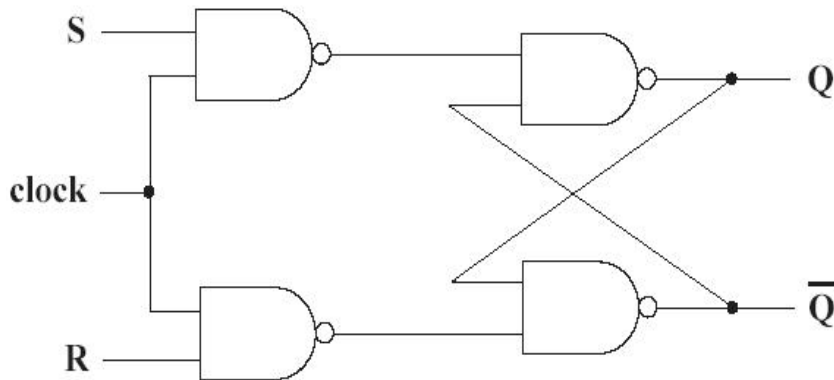


Truth table

CLK	S	R	Comment
1	0	0	Hold
1	1	0	Set
1	0	1	Reset
1	1	1	Invalid

2
1

38. Block diagram of OFC

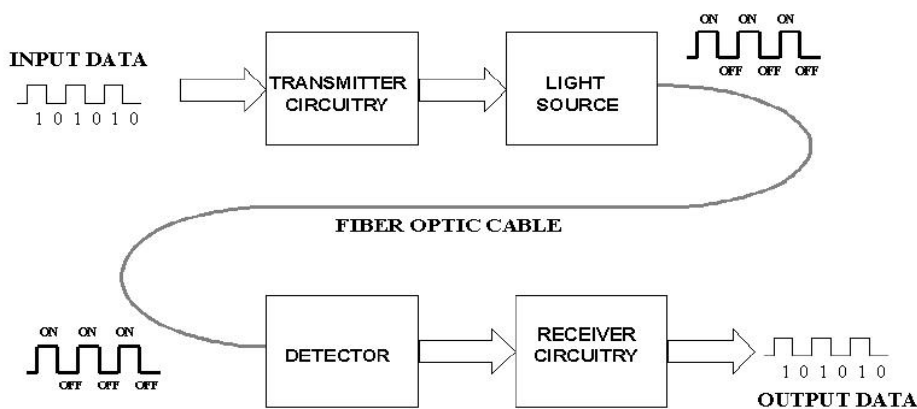

Any two application

- (i) Used to achieve high speed data communication
- (ii) To achieve errorless far distance communication.

1
2



PART D

V Any five of the following

5x5 = 25


39. Circuit diagram with wave form.

2

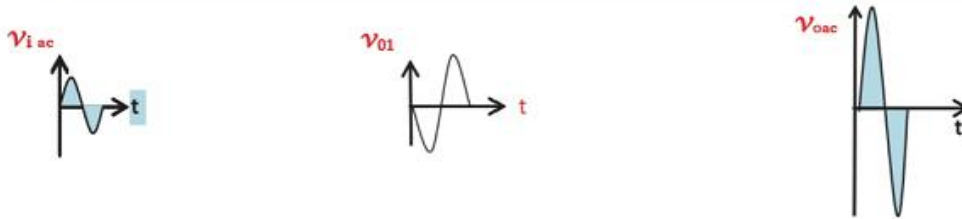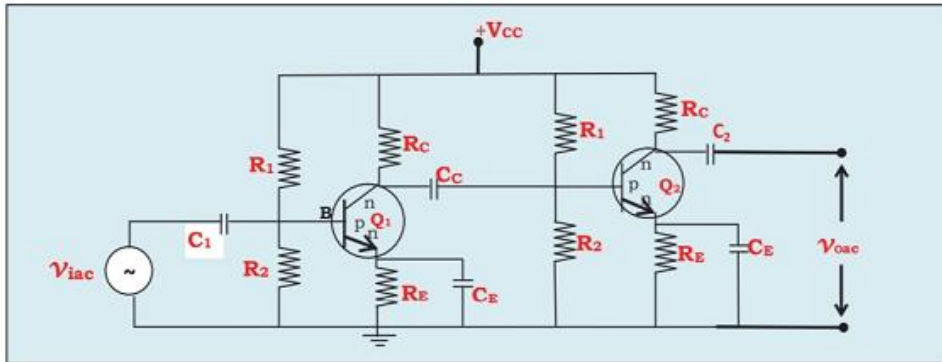

Frequency Response Curve:

1

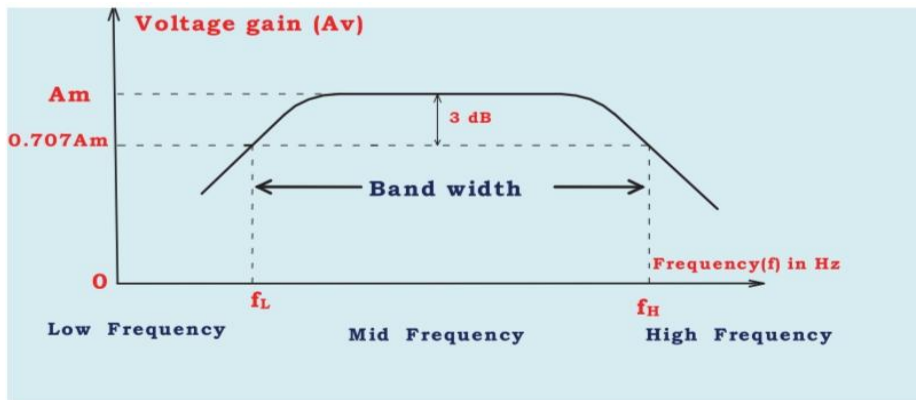


Working

2

40. Circuit diagram :

1

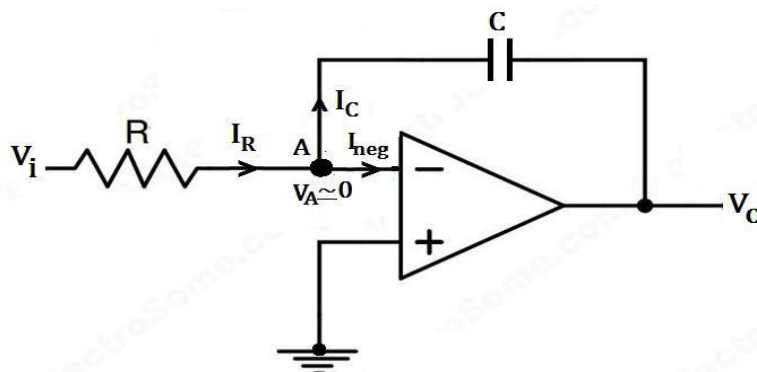

Steps Applying KCL and node

1

Rearranging $i = \frac{dq}{dt}$

1

Replacing $q = cv$, rearranging equation

Integrating on both sides

Arriving output expression $V_0 = \frac{1}{RiC} \int Vi dt$

1

1

41. Any five difference between AM and FM


(each 1 M)

5

Amplitude modulation	Frequency modulation
It is a process in which amplitude of the carrier varied in accordance with instantaneous voltage of the modulating signal.	It is a process in which frequency of the carrier varied in accordance with instantaneous voltage of the modulating signal.
It has only two side bands	It has infinite side bands
Area of reception is large	Area of reception is smaller than AM and which is limited to LOS
Bandwidth is very less (10KHz)	Bandwidth is very high (200KHz)
Modulation index will be less than 1	Modulation index will be greater than 1

42. Pin diagram of NOR (IC 7402)

1

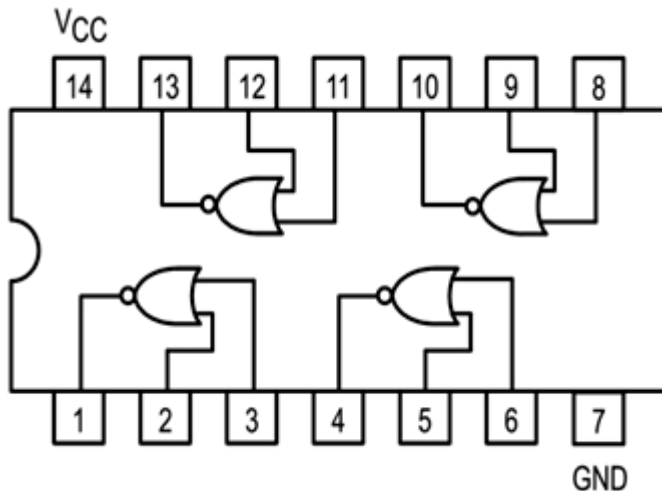

Constructing NOT gate & truth table
 Constructing AND gate & truth table
 Constructing OR gate & truth table
 Constructing XNOR gate & truth table

1
1
1
1

43. ALP to standard two hex numbers

CLR C : Clear carry
 MOV, #78H : Load 78H to A
 SUBB A, #4CH : Subtract 4CH from 78H
 MOV R₀, A : Store difference in R₀

Verification:
 A : 78H 0111 1000 → 0111 1000
 R1: 4CH 0110 1100 → 1011 0011
 + 1
 0010 1100

1
1
1
1
1

<p>44.</p>	<pre># include <stdio.h> Void main() { int p, q, r, s, sum; float avg; printf("Enter the four integer number\n"); scanf("%d %d %d %d", &p, &q,&r, &s); sum = p + q + r + s; avg = sum/4; printf("sum = %d\n avg = %f\n, sum, avg); }</pre>	
<p>45.</p>	<p>Transistor CE Amplifier Given $R_1 = 45k\Omega$, $R_2 = 5k\Omega$, $R_C = 10k\Omega$, $R_E = 1k\Omega$ $I_E = 1.3mA$, $\beta = 100$</p> $I_E = \frac{26mV}{r'_e} = r'_e = \frac{26 \times 10^{-3}}{1.3 \times 10^{-3}} = 20\Omega$ $Z_0 = R_C \parallel R_L = \frac{10k \cdot 10k}{10k + 10k} = 5k\Omega$ $A_V = -\frac{z_o}{r'_e} = \frac{5 \times 10^3}{20} = -250$ $A_i = \beta = 100$ $A_P = A_V \cdot A_i = 250 \times 100 = 25000$	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p>
<p>46.</p>	<p>Stage 1: OP-AMP Subtractor</p> $V_0 = \frac{V_2 R_3}{R_2 + R_3} \left[1 + \frac{R_f}{R_1} \right] - \frac{R_f}{R} (V_{0_1})$ <p>Or $V_{01} = V_2 - V_1$</p> $V_{0_1} = 8mV - 2mV = 6mV$ <p>Stage 2: OP-AMP inverting amplifier</p> $V_0 = -\frac{R_f}{R} (V_1)$ $= \frac{-6 \times 10^3}{3 \times 10^3} (6 \times 10^{-3})$ $V_0 = -12 mV$	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p>

47.

Given $m_a = 75\% = 0.75$

$P_C = 12\text{kW}$

$P_T = ?$

$P_{S\beta} = ?$

$$P_T = P_C \left[1 + \frac{m_a^2}{2} \right]$$

$$P_T = 12 \times 10^3 \left[1 + \frac{(0.75)^2}{2} \right]$$

$$P_T = 12 \times 10^3 [1 + 0.281]$$

$$P_T = 15.37\text{kW}$$

$$P_T = P_C + P_{S\beta}$$

$$P_{S\beta} = P_T - P_C$$

$$= 15.37 \times 10^3 - 12 \times 10^3$$

$$P_{S\beta} = 3.37\text{kW}$$

Each side hand $P_{LS\beta} = P_{US\beta} = \frac{P_{S\beta}}{2}$

$$P_{LS\beta} = P_{US\beta} = \frac{3.37 \times 10^3}{2} = 1.68\text{kW}$$

1

1


1

1

1

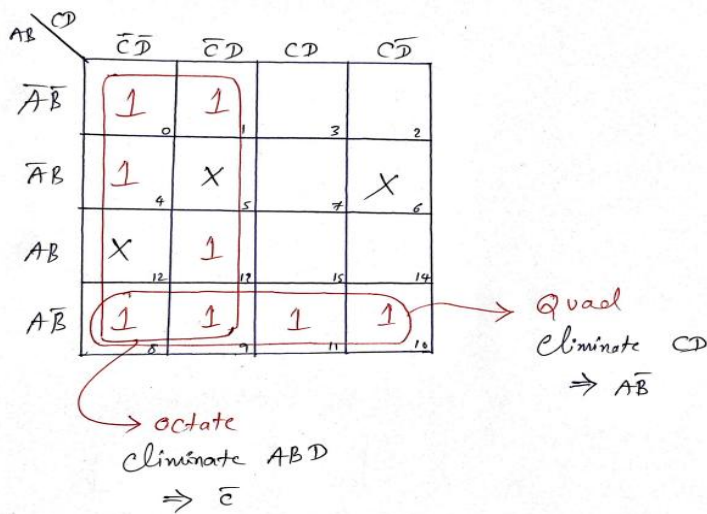48.

$$y = \sum m(0, 1, 4, 8, 9, 10, 11, 13) + \sum d(5, 6, 12)$$




$$y = \bar{C} + A\bar{B}$$

→ 4M

4

Simplified expression using NAND only

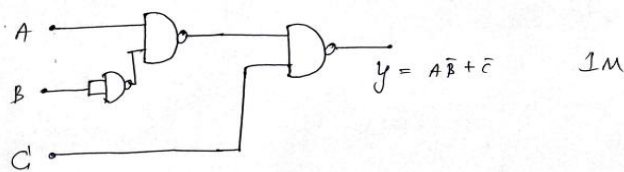

1M

1